
 


P1

 

```
 1 module moore10110 (input clk, rst, j , output w);
 2     reg [2:0] ns,ps;
 3
 4     parameter [2:0] A=3'b000 , B=3'b001 , C=3'b010 ,
 5     D=3'b011, E=3'b100 , F=3'b101;
 6
 7     always @(j,ps) begin
 8         ns=A;
 9         case (ps)
10             A: ns= j ? B : A;
11             B: ns= j ? B : C;
12             C: ns= j ? D : A;
13             D: ns= j ? E : C;
14             E: ns= j ? B : F;
15             F: ns= j ? D : A;
16             default: ns=A;
17         endcase
18     end
19
20     assign w = (ps==F) ? 1'b1 : 1'b0;
21
22     always @ (posedge clk , posedge rst) begin
23         if(rst) ps<=3'b000;
24         else ps<=ns;
25     end
26 endmodule
```

Table of Contents

### Analysis & Synthesis Summary

<<Filter>>

Analysis & Synthesis Status	Successful - Tue Dec 30 07:51:22 2025
Quartus Prime Version	20.1.0 Build 711 06/05/2020 SJ Lite Edition
Revision Name	moore10110
Top-level Entity Name	moore10110
Family	Cyclone IV GX
Total logic elements	5
Total registers	5
Total pins	4
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total GXB Receiver Channel PCS	0
Total GXB Receiver Channel PMA	0
Total GXB Transmitter Channel PCS	0
Total GXB Transmitter Channel PMA	0
Total PLLs	0

Timing Analyzer - C:/Users/Asus/Desktop/university/term 3/logic circuit/CA/CA5/moore10110 - moore10110

File View Netlist Constraints Reports Script Tools Window Help

Search altera.com

Set Operating Conditions

- Slow 1200mV 125C Model
- Slow 1200mV -40C Model
- Fast 1200mV -40C Model

Report

- Timing Analyzer Summary
- Advanced I/O Timing

Tasks

- Open Project...
- Netlist Setup
- Create Timing Netlist
- Read SDC File

Timing Analyzer Summary


Quartus Prime Version	Version 20.1.0 Build 711 06/05/2020 SJ Lite Edition
Timing Analyzer	Legacy Timing Analyzer
Revision Name	moore10110
Device Family	Cyclone IV GX
Device Name	EP4CGX15BF14A7
Timing Models	Final
Delay Model	Slow 1200mV 125C Model
Rise/Fall Delays	Enabled

Console


```
tcl> Synopsys Design Constraints File file not found: 'moore10110.sdc'. A Synopsys Design C
tcl> tcl update_timing_netlist
tcl> ① No user constrained base clocks found in the design. Calling "derive_clocks -period 1.
tcl> ① Deriving Clocks
tcl> ① No user constrained clock uncertainty found in the design. Calling "derive_clock_uncer
tcl> ① Deriving Clock Uncertainty. Please refer to report_sdc in the Timing Analyzer to see c
```

Console / History /


## Floorplan

 



## Post mapping

 



## Post fitting

 

  Waveforms of pre&post synthesize moore machine



P2

  


```
1 module mealy10110(input clk, rst, j , output w);
2     reg [2:0]ns,ps;
3     parameter [2:0] A=3'b000, B=3'b001, C=3'b010,
4     D=3'b011 , E=3'b100;
5
6     always @(ps, j) begin
7         ns=A;
8         case (ps)
9             A: ns= j ? B : A;
10            B: ns= j ? B : C;
11            C: ns= j ? D : A;
12            D: ns= j ? E : C;
13            E: ns= j ? B : C;
14            default: ns=A;
15        endcase
16    end
17
18    assign w = (ps==E && j==1'b0) ? 1'b1 : 1'b0;
19
20    always @(posedge clk, posedge rst) begin
21        if(rst) ps<=A;
22        else ps<=ns;
23    end
24
25 endmodule
```

Table of Contents


**Analysis & Synthesis Summary**

<<Filter>>	
Analysis & Synthesis Status	Successful - Tue Dec 30 07:56:37 2025
Quartus Prime Version	20.1.0 Build 711 06/05/2020 SJ Lite Edition
Revision Name	mealy10110
Top-level Entity Name	mealy10110
Family	Cyclone IV GX
Total logic elements	5
Total registers	4
Total pins	4
Total virtual pins	0
Total memory bits	0
Embedded Multiplier 9-bit elements	0
Total GXB Receiver Channel PCS	0
Total GXB Receiver Channel PMA	0
Total GXB Transmitter Channel PCS	0
Total GXB Transmitter Channel PMA	0
Total PLLs	0


As we can see the Mealy machine uses four registers while the Moore machine uses five. This is because a **Moore** machine requires an additional state to represent the detection of the sequence, since its output depends only on the current state. In contrast, the **Mealy** machine output depends on both the present state and the current input. Therefore, instead of the last register in moore we can use an AND gate between the state condition and the input.

 


'qu2/mealy10110 - mealy10110

 


## Post mapping

 


## Post fitting

 

 Waveforms of pre&post synthesize mealy machine



P3

 

## Testbench (which apply to all parts)

```
1 `timescale 1ns/1ns
2 module compare_TB ();
3   reg clk, rst, j;
4   wire moore,mealy;
5   moore10110_post instant(.clk(clk) , .rst(rst) , .j(j) , .w(moore));
6   mealy10110_post instantt(.clk(clk) , .rst(rst) , .j(j) , .w(mealy));
7   initial begin
8     clk=1'b0; #100;
9     forever begin
10       clk = ~clk; #100;
11     end
12   end
13
14   initial begin
15     rst = 1'b0;
16     j=1'b0; #220;
17     j=1'b1; #200;
18     j=1'b0; #220;
19     j=1'b1; #300;
20     j=1'b0; #100;
21     j=1'b1; #20;//for mealy
22     j=1'b0; #100;
23     j=1'b1; #350;
24     j=1'b0; #220;
25     rst=1'b1; #20;
26     $finish;
27   end
28 endmodule
```